

Q.1 Answer any 5 questions (5*1=5)

1.a The resistance is high in case of ____ (metal/semiconductor /insulators) 1.b Which of the digital gates are known as the special purpose gates? 1.c An ideal voltage source has internal resistance value ____ . 1.d Given dc source, an inductor works as ____ circuit.(short/open) 1.e The decimal equivalent of binary $(11011)_2$ is ____ . 1.f p type semiconductor is electrically ____ (positive/negative/neutral) 1.g To convert the type of intrinsic semiconductor into p type extrinsic semiconductor, ____ type of dopant element should be added to it.


Q.2 Answer any 3 questions (5*3=15)

2.a With a neat diagram, explain the band diagram structure of metal, semiconductor and insulator. Show the formation of a PN junction diode with a proper diagram. 2.5+2.5

2.b What is intrinsic and extrinsic semiconductor? Draw the current-voltage characteristics of the PN diode in forward and reverse bias mode. 2.5+2.5

2.c Draw the truth table of a XOR gate and write down the logical expression of it. How can you construct an AND gate using NOR gates only (using De Morgan law)? 2.5+2.5

2.d How can you convert a practical current source to a voltage source? Find the value of current i in the following figure using source transformation 1+4

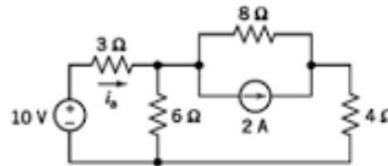**Q.1 Answer any 5 questions (5*1=5)**

1.a The resistance is high in case of ____ (metal/semiconductor /insulators) 1.b Which of the digital gates are known as the special purpose gates? 1.c An ideal voltage source has internal resistance value ____ . 1.d Given dc source, an inductor works as ____ circuit.(short/open) 1.e The decimal equivalent of binary $(11011)_2$ is ____ . 1.f p type semiconductor is electrically ____ (positive/negative/neutral) 1.g To convert the type of intrinsic semiconductor into p type extrinsic semiconductor, ____ type of dopant element should be added to it.

Q.2 Answer any 3 questions (5*3=15)

2.a With a neat diagram, explain the band diagram structure of metal, semiconductor and insulator. Show the formation of a PN junction diode with a proper diagram. 2.5+2.5

2.b What is intrinsic and extrinsic semiconductor? Draw the current-voltage characteristics of the PN diode in forward and reverse bias mode. 2.5+2.5

2.c Draw the truth table of a XOR gate and write down the logical expression of it. How can you construct an AND gate using NOR gates only (using De Morgan law)? 2.5+2.5

2.d How can you convert a practical current source to a voltage source? Find the value of current i in the following figure using source transformation 1+4

